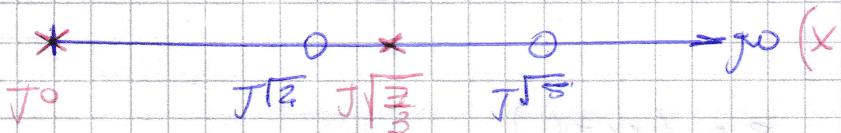


$$2) \frac{Y(s)}{Z(s)} = \frac{3 \cdot s \cdot (s^2 + \frac{7}{3})}{(s^2+2)(s^2+5)}$$

$$\frac{Z(s)}{Y(s)} = \frac{1}{\frac{(s^2+2)(s^2+5)}{3 \cdot s \cdot (s^2 + \frac{7}{3})}}$$



Realizamos una remoción parcial del polo en continua para obtener un cero en  $\omega = 1$ .

$$K'_0 = \left. \frac{Z(s)}{Y(s)} \cdot s \right|_{s=J1}$$

$$K'_0 = \left. \frac{(s^2+2)(s^2+5)}{3 \cdot s \cdot (s^2 + \frac{7}{3})} \cdot s \right|_{s=J1} = ①.$$

De lo tanto,  $C_1 = 1$ .

$$Z_2(s) = Z(s) = \frac{k'_0}{s} = \frac{(s^2+2)(s^2+5)}{3 \cdot s \cdot (s^2 + \frac{7}{3})} = \frac{s^4 + 4s^2 + 3}{3 \cdot s \cdot (s^2 + \frac{7}{3})}$$

$$Y_2(s) = \frac{3 \cdot s \cdot (s^2 + \frac{7}{3})}{s^4 + 4s^2 + 3}$$

$$2 \cdot K'_1 = Y_2(s) \cdot \left. \frac{s^2+1}{s} \right|_{s=J1} = \frac{3 \cdot s \cdot (s^2 + \frac{7}{3}) \cdot (s^2+1)}{s^4 + 4s^2 + 3} \Big|_{s=J1}$$

$$= \frac{3 \cdot s \cdot (s^2 + \frac{7}{3}) \cdot \left. \frac{s^2+1}{s} \right|_{s=J1}}{(s^2+1)(s^2+3)} = \frac{3 \cdot (s^2 + \frac{7}{3})}{s^2+3} \Big|_{s=J1} = 2$$

$$(K_1') = 1$$

Se remueve una de las resistencias en la red en  $\mathcal{Z}^1$ .

$$C_2 = \frac{2 K_1'}{\omega_1^2} = 2$$


$$L_2 = \frac{1}{2 K_1'} = \frac{1}{2}$$

Para la otra red:

$$\begin{aligned} Y_4(s) &= Y_2(s) - \frac{2s}{s^2+1} = \frac{3s(s^2 + 7/3)}{(s^2+1)(s^2+3)} - \frac{2s}{s^2+1} \\ &= \frac{1}{s^2+1} \cdot \left( \frac{3s(s^2 + 7/3)}{s^2+3} - 2s \right) \end{aligned}$$

$$\begin{aligned} Y_4(s) &= \frac{1}{s^2+1} \cdot \left( \frac{3s(s^2 + 7/3) - 2s(s^2+3)}{s^2+3} \right) \\ &= \frac{1}{s^2+1} \cdot \frac{s^3 + s}{s^2+3} = \frac{1}{s^2+1} \cdot \frac{s(s^2+1)}{s^2+3} = \frac{s}{s^2+3} = \frac{1}{\frac{s^2+3}{s}} \end{aligned}$$
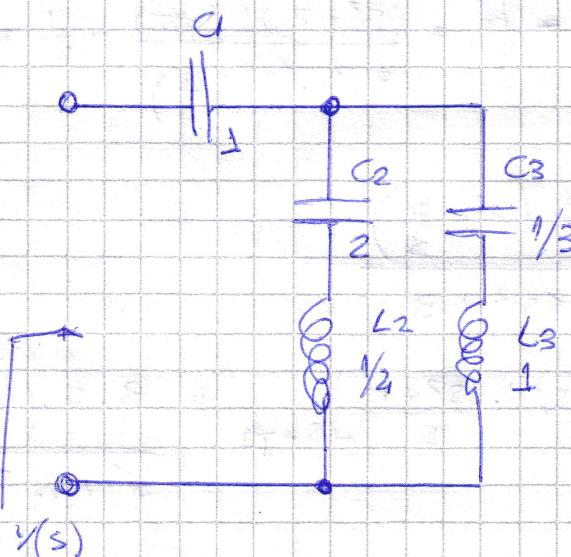
$$= \frac{1}{s^2 + \frac{1}{\frac{1}{3} \cdot s}}$$



$$\boxed{C_3 = \frac{1}{3}} \quad \cap \quad \boxed{L_3 = 1}$$

NOTA