

1) B) Círculo ② (Relevación de polos en $w = 0$)

$$Z(s) = \frac{(s^2+3)(s^2+1)}{s(s^2+2)}$$




$$Z_2(s) = \frac{(s^2+3)(s^2+1)}{s(s^2+2)} - \frac{k_0}{s}$$

$$k_0 = \lim_{s \rightarrow 0} s \cdot Z(s) = \lim_{s \rightarrow 0} \frac{(s^2+3)(s^2+1)}{s(s^2+2)}, \cancel{s} = \frac{3}{2}$$

$$\frac{k_0}{s} = \left(\frac{2 \cdot s}{3} \right) \underset{s \rightarrow 0}{\cancel{s}} = \text{Coeficiente el primer término de } \frac{2}{3}$$
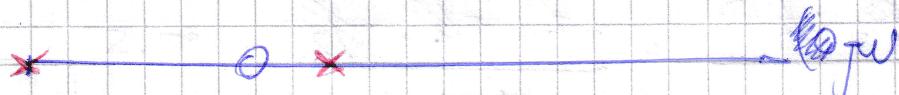
$$Y_2(s) = \frac{1}{Z_2(s)} = \frac{s(s^2+2)}{s^4 + \frac{5}{2}s^2}$$



$$Y_4(s) = \frac{s(s^2+2)}{s^4 + \frac{5}{2}s^2} - \frac{k_{01}}{s} = \frac{s^3 + 2s - \frac{k_{01}}{s} \left(s^4 + \frac{5}{2}s^2 \right)}{s^4 + \frac{5}{2}s^2}$$


$$k_{01} = \lim_{s \rightarrow 0} s \cdot Y_4(s) = \lim_{s \rightarrow 0} \frac{s^2(s^2+2)}{s^4 + \frac{5}{2}s^2} = \frac{4}{5}$$

$$\frac{k_{01}}{s} = \left(\frac{4}{5} \right) \underset{s \rightarrow 0}{\cancel{s}} = Y_4(s)$$

representa un ~~expresión~~ en derivadas de orden $\frac{4}{5}$

$$Y_3(s) = \frac{\frac{1}{5} \cdot s^3}{s^4 + \frac{5}{2} \cdot s^2}$$
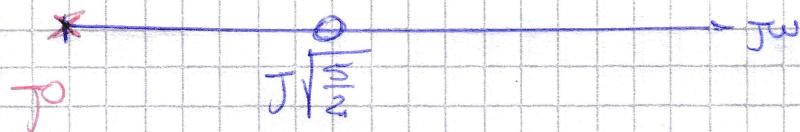
$$Z_2(s) = \frac{s^4 + \frac{5}{2}s^2}{s^3} \rightarrow \frac{s^2 + 5/2}{s}$$



$$Z_0(s) = \frac{s^2 + 5/2}{\frac{1}{5} \cdot s} - \frac{k_{02}}{s} = \frac{s^2 + 5/2 - \frac{k_{02}}{s} \cdot \frac{1}{5} s}{\frac{1}{5} \cdot s}$$

$$k_{02} = \lim_{s \rightarrow 0} Z_0(s) \cdot s = \lim_{s \rightarrow 0} \frac{s^2 + 5/2 - \frac{k_{02}}{s} \cdot \frac{1}{5} s}{\frac{1}{5} \cdot s} \cdot \left(0 + \frac{5}{2}\right) = \frac{25}{2}$$

$\frac{k_{02}}{s}$ representa un capacitor en serie de valor $\left(\frac{2}{25}\right)$.

$$Z_0(s) = \frac{s^2 + 5/2 - \frac{25}{2 \cdot s} \cdot \frac{1}{5} s}{\frac{1}{5} \cdot s} = \frac{s^2 + 5/2 - 25/2}{\frac{1}{5} \cdot s} = 5 \cdot s.$$

$5 \cdot s$ representa un inductor en derivación de valor (s) .

